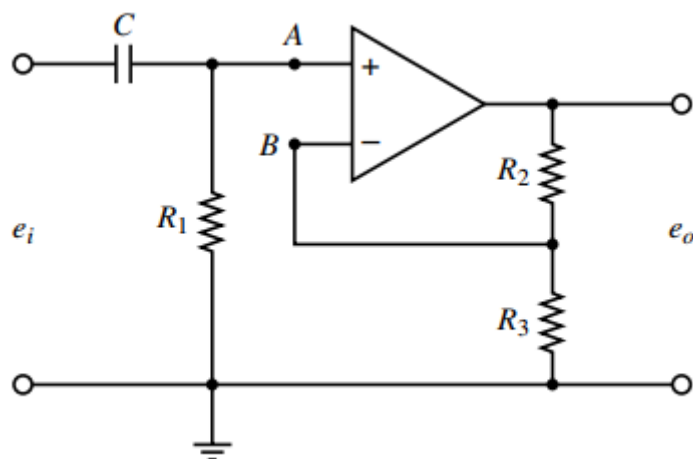


Name:

ID#:

### Problem 1


Obtain the transfer function  $E_o(s)/E_i(s)$  of the op-amp circuit.



**Solution**

## Problem 2

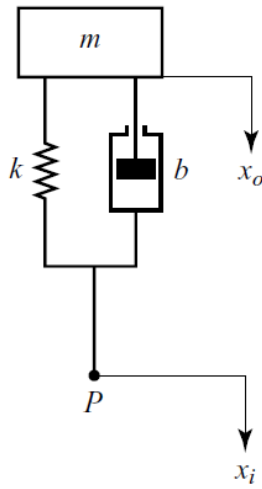- A. For the following mechanical system, prove that  $G_{(s)} = \frac{x_{o(s)}}{x_{i(s)}} = \frac{bS+K}{(mS^2+bS+K)}$
- B. As well as draw the Free Body Diagram.



**Solution**